

CHAPTER 7

Alternating Current

Mean Value and Virtual Value of A.C.


- The peak voltage of the ac source is equal to (2022)
 - $\frac{1}{\sqrt{2}}$ times the rms value of the source
 - the value of voltage supplied to the circuit
 - the rms value of the ac source
 - $\sqrt{2}$ times the rms value of the ac source

A.C. Circuit Containing Capacitance Only

- A capacitor of capacitance 'C', is connected across an ac source of voltage V, given by $V = V_0 \sin \omega t$. The displacement current between the plates of the capacitor, would then be given by: (2021)
 - $I_d = \frac{V_0}{\omega C} \cos \omega t$
 - $I_d = \frac{V_0}{\omega C} \sin \omega t$
 - $I_d = V_0 \omega C \sin \omega t$
 - $I_d = V_0 \omega C \cos \omega t$
- A 40 μF capacitor is connected to a 200V, 50Hz ac supply. The rms value of the current in the circuit is, nearly: (2020)
 - 2.05 A
 - 2.5 A
 - 25.1 A
 - 1.7 A
- A small signal voltage $V(t) = V_0 \sin \omega t$ is applied across an ideal capacitor C : (2016 - I)
 - Current I(t) lags voltage V(t) by 90°
 - Over a full cycle the capacitor C does not consume any energy from the voltage source
 - Current I(t) is in phase with voltage V(t)
 - Current I(t) leads voltage V(t) by 180°

A.C. Circuit Containing R and L Only

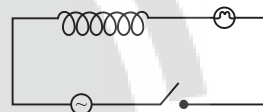- A light bulb and an inductor coil are connected to an ac source through a key as shown in the figure below. The key is closed and after sometime an iron rod is inserted into the interior of the inductor. The glow of the light bulb (2020-Covid)



- Remains unchanged
 - Will fluctuate
 - Increases
 - Decreases
- A resistance R draws power P when connected to an AC source. If an inductance is now placed in series with the resistance, such that the impedance of the circuit becomes Z, the power drawn will be: (2015)
 - $P \sqrt{\frac{R}{Z}}$
 - $P \left(\frac{R}{Z} \right)$
 - P
 - $P \left(\frac{R}{Z} \right)^2$
 - A coil of self-inductance L is connected in series with a bulb B and an AC source. Brightness of the bulb decreases when: (2013)
 - An iron rod is inserted in the coil
 - Frequency of the AC source is decreased
 - Number of turns in the coil is reduced
 - A capacitance of reactance $X_C = X_L$ is included in the same circuit

A.C. Circuit Containing R and C Only


- A series RC circuit is connected to an alternating voltage source. Consider two situations
 - When capacitor is air filled.
 - When capacitor is mica filled.

Current through resistor is i and voltage across capacitor is V then:
(2015 Re)


- a. $V_a = V_b$ b. $V_a < V_b$
c. $V_a > V_b$ d. $I_a > I_b$

A.C. Circuit Containing R, L and C

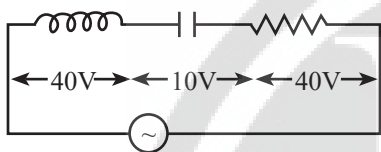9. An inductor of inductance L , a capacitor of capacitance C and a resistor of resistance ' R ' are connected in series to an ac source of potential difference ' V ' volts as shown in figure. Potential difference across L , C and R is 40V, 10V and 40V, respectively. The amplitude of current flowing through LCR series circuit is $10\sqrt{2}$ A. The impedance of the circuit is:
(2021)



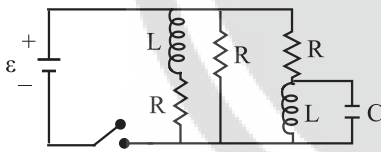- a. $5/\sqrt{2} \Omega$ b. 4Ω
c. 5Ω d. $4\sqrt{2} \Omega$
10. Figure shows a circuit that contains three identical resistors with resistance $R = 9.0 \Omega$ each, two identical inductors with inductance $L = 2.0$ mH each, and an ideal battery with emf $\varepsilon = 18$ V. The current ' i ' through the battery just after the switch closed is:
(2017-Delhi)



- a. 0.2 A b. 2 A
c. 0 ampere d. 2 mA

Electric Resonance

11. A series LCR circuit with inductance 10 H, capacitance 10 μ F, resistance 50 Ω is corrected to an ac source of voltage, $V = 200 \sin(100t)$ volt. If resonant frequency of the LCR circuit is ν_0 and the frequency of the ac source is ν , then:
(2022)

- a. $\nu = 100\text{Hz}; \nu_0 = \frac{100}{\pi} \text{Hz}$
b. $\nu_0 = \nu = 50 \text{Hz}$
c. $\nu_0 = \nu = \frac{50}{\pi} \text{Hz}$
d. $\nu_0 = \frac{50}{\pi} \text{Hz}, \nu = 50\text{Hz}$

12. A series LCR circuit is connected to an ac voltage source. When L is removed from the circuit, the phase difference between current and voltage is $\frac{\pi}{3}$. If instead C is removed from the circuit, the phase difference is again $\frac{\pi}{3}$ between current and voltage. The power factor of the circuit is:
(2020)

- a. 0.5 b. 1.0
c. -1.0 d. Zero

13. Which of the following combinations should be selected for better tuning of an L-C-R circuit used for communication?
(2016 - II)

- a. $R = 15 \Omega, L = 3.5 \text{ H}, C = 30 \mu\text{F}$
b. $R = 25 \Omega, L = 1.5 \text{ H}, C = 45 \mu\text{F}$
c. $R = 20 \Omega, L = 1.5 \text{ H}, C = 35 \mu\text{F}$
d. $R = 25 \Omega, L = 2.5 \text{ H}, C = 45 \mu\text{F}$

Average Power and Power Associated with A.C. Circuits and Power Factor

14. A series LCR circuit containing 5.0 H inductor, 80 μ F capacitor and 40 Ω resistor is connected to 230 V variable frequency ac source. The angular frequencies of the source at which power transferred to the circuit is half the power at the resonant angular frequency are likely to be:
(2021)

- a. 50 rad/s and 25 rad/s
b. 46 rad/s and 54 rad/s
c. 42 rad/s and 58 rad/s
d. 25 rad/s and 75 rad/s

15. An inductor 20mH, a capacitor 100 μ F and a resistor 50 Ω are connected in series across a source of emf, $V = 10 \sin 314 t$. The power loss in the circuit is
(2018)

- a. 2.74 W b. 0.43 W
c. 0.79 W d. 1.13 W

16. The potential differences across the resistance, capacitance and inductance are 80 V, 40 V and 100 V respectively in an LCR circuit. The power factor of this circuit is:
(2016 - II)

- a. 0.8 b. 1.0
c. 0.4 d. 0.5

17. An inductor 20 mH, a capacitor 50 μ F and a resistor 40 Ω are connected in series across a source of emf $V = 10 \sin 340t$. The power loss in A.C. circuit is:
(2016 - I)

- a. 0.51 W b. 0.67 W
c. 0.76 W d. 0.89 W

a. 300 V, 15 A
b. 450 V, 15 A
c. 450 V, 13.5 A
d. 600 V, 15 A

[illegible]