

# Alternating Current

- ❖ The constant value of dc which produces same heat through a resistive element, as due to the alternating current, is known as root mean square value of ac.
- ❖ 240 V ac is the rms value of ac voltage. The amplitude of this voltage is  $V_M = 240 \times \sqrt{2} \approx 340$  volt.
- ❖ The power rating in ac circuit is the average power rating.
- ❖ Power consumed in a circuit is non negative.
- ❖ Phase relationships in a.c. circuits is best represented by phasor diagram. A phasor is a vector which rotates with the angular velocity  $\omega$ . The magnitude of phasor is the peak value of voltage or current ( $V_o$  or  $I_o$ ).
- ❖ In purely resistive AC circuit, voltage and current are in the same phase  $V = V_o \sin \omega t$  and  $I = I_o \sin \omega t$ , where  $I_o = \frac{V_o}{R}$ .
- ❖ In purely resistive circuit, average power loss  $= I_{rms}^2 \times R$ ,  $I_{rms} = \frac{I_o}{\sqrt{2}}$ , similarly  $V_{rms} = \frac{V_o}{\sqrt{2}}$
- ❖ The only element which dissipates energy in ac circuit is resistor (R).
- ❖ In purely inductive circuit, inductive reactance  $X_L = 2\pi fL = \omega L$ . Voltage is ahead of current by  $\frac{\pi}{2}$ ,  $V = V_o \sin \omega t$ ,  $I = I_o \sin\left(\omega t - \frac{\pi}{2}\right)$ ,  $I_o = \frac{V_o}{X_L}$ . In this circuit, average power loss = 0.
- ❖ In purely inductive or capacitive circuit,  $\cos \phi = 0 \Rightarrow \phi = \frac{\pi}{2}$ .  
Average power loss is zero. Although current is flowing in the circuit. Such a current is known as wattless current.
- ❖ In AC L-R circuit, total voltage  $V = \sqrt{V_R^2 + V_L^2}$ .
- ❖ In purely capacitive AC circuit, capacitive reactance  $X_C = \frac{1}{2\pi fC} = \frac{1}{\omega C}$ . The current leads the applied voltage by  $\frac{\pi}{2}$  or  $90^\circ$ .  $V = V_o \sin \omega t$ ,  $I = I_o \sin\left(\omega t + \frac{\pi}{2}\right)$ ,  $I_o = \frac{V_o}{X_C} = 2\pi fCV_o$ . The average power loss per cycle is zero.
- ❖ In AC C-R circuit, total voltage  $V = \sqrt{V_R^2 + V_C^2}$ .
- ❖ A circuit containing an inductor L and a capacitor C (initially charged) with no ac source and no resistors, exhibits free oscillations. The charge of the capacitor is given by the differential equation  $\frac{d^2q}{dt^2} + \frac{1}{LC}q = 0$ . The sum of energy of capacitor and inductor is constant.
- ❖ For a given RLC circuit driven by voltage  $V = V_o \sin \omega t$ , the current is given by,  $I = I_o \sin(\omega t + \phi)$  where  $I_o = \frac{V_m}{\sqrt{R^2 + (X_C - X_L)^2}}$  and  $\phi = \tan^{-1} \frac{X_C - X_L}{R}$ , impedance  $z = \sqrt{R^2 + (X_C - X_L)^2}$ .
- ❖ The phase difference between voltage across L and voltage across capacitor C, is  $180^\circ$ . Thus  $V_{LC} = V_L - V_C$ .
- ❖ The voltage in series LCR AC circuit is given by  $V = \sqrt{V_R^2 + (V_L - V_C)^2}$ .
- ❖ The average power consumed  $= V_{rms} \times I_{rms} \times \cos \phi$ , where  $\cos \phi$  is the power factor.
- ❖ In series LCR circuit, at resonance,  $X_L = X_C$ , the impedance Z is minimum and equal to R. In this case, the source frequency  $\omega = \frac{1}{\sqrt{LC}}$  which equals resonant frequency.
- ❖ The quality factor  $Q = \omega_0 \frac{L}{R} = \frac{1}{\omega_0 CR} = \frac{1}{R} \sqrt{\frac{L}{C}}$  is an indicator or “sharpness of resonance.”
- ❖ The power factor in a RLC circuit is a measure of how close the circuit is to consuming maximum power.

- ❖ A step up transformer converts low ac voltage to high ac voltage but reduces the current.
- ❖ A step down transformer converts high ac voltage to a low ac voltage but increases the current accordingly.
- ❖ In transformer, the primary and secondary voltage are given by  $V_S = \left(\frac{N_S}{N_P}\right)V_P$  and the current are given by  $I_S = \left(\frac{N_P}{N_S}\right)I_P$ .

In step up transformer,  $N_S > N_P$  and step down transformer  $N_S < N_P$ .

- ❖ A generator converts mechanical energy into electrical energy, whereas an electric motor converts electrical energy into mechanical energy.
- ❖ A transformer does not violate the law of conservation of energy. A step up transformer changes low voltage to a high voltage but reduces the current in the same proportion.